

Convert the following:-

(a) Decimal to binary $\rightarrow (34.4375)_{10}$

Sols:-

$$\begin{array}{r} 34 \\ \hline 2 | 17 - 0 \\ 2 | 8 - 1 \\ 2 | 4 - 0 \\ 2 | 2 - 0 \\ 1 - 0 \end{array}$$

4375

0x4375

$0.4375 \times 2 = 0.5$

$0.875 \times 2 = 1.7$

$$34 = 100010 \quad (100010.01)_2$$

(b) $(10110.0101)_2$ Binary fraction to decimal AND

Sols:-

$$10110 = 0 \times 2^0 + 1 \times 2^1 + 1 \times 2^2 + 0 \times 2^3 + 1 \times 2^4$$

$$\begin{aligned} 10110 &= 0 + 2 + 4 + 0 + 16 \\ &= 22 \end{aligned}$$

$$\begin{aligned} 0101 &= 0 \times 2^{-1} + 1 \times 2^{-2} + 0 \times 2^{-3} + 1 \times 2^{-4} \\ &= 0 + \frac{1}{4} + 0 + \frac{1}{16} \\ &= \frac{4+1}{16} \\ &= \frac{5}{16}, \\ &= 0.3125 \end{aligned}$$

$$(10110.0101)_2 \rightarrow (22.3125)_{10}$$

(c) $(26.24)_8$ octal to binary.

Sols:-

$$\text{octal} = 2^3;$$

$$\text{Binary} = 2^1;$$

$\frac{2}{\downarrow}$	6	.	2	4
010	110	.	010	100

$$\therefore (26.24)_8 \rightarrow (010110.010100)_2$$

(d) $(1110.10)_2 \rightarrow$ Binary to decimal.

Sol:-

$$\begin{aligned} &= 0 \times 2^0 + 1 \times 2^1 + 1 \times 2^2 + 1 \times 2^3 + 1 \times 2^{-1} + 0 \times 2^{-2} \\ &= 0 + 2 + 4 + 8 + \frac{1}{2} + 0 \\ &= 14 + \cancel{\frac{1}{2}}^{0.5} \\ &= 14.5 \\ &(1110.10)_2 \rightarrow (14.5)_{10} \end{aligned}$$

(2) Add Binary number 1011 and 101

Sol:-

$$\begin{array}{r} \textcircled{1} \textcircled{0} \textcircled{1} \\ 1011 \\ + 101 \\ \hline 10000 \end{array}$$

(3) Find 9's and 10's Complement of the decimal

(9) 98127634.

Sol:- Let, $n = 98127634$

Subtract 'n' from '9'. We get 9's Complement of the decimal.

$$\begin{array}{r} 99999999 \\ - 98127634 \\ \hline 01872365 \end{array}$$

\therefore 9's Complement = 1872365.

10's Complement = 9's Complement + 1
= add '1' to 9's Complement.

$$\begin{array}{r} 1872365 \\ + 1 \\ \hline 1872366 \end{array}$$

\therefore 10's Complement = 1872366.

(ii) 72049900
 Sol:- Let, $n = 72049900$
 subtract 'n' from '9'. we get 9's Complement
 of the decimal.

$$\begin{array}{r} 99999999 \\ 72049900 \\ \hline 27950099 \end{array}$$

\therefore 9's Complement = 27950099

10's Complement = 9's Complement + 1

$$\begin{array}{r} 27950099 \\ + 1 \\ \hline 27950100 \end{array}$$

10's Complement = 27950100

(4) Find 1's and 2's Complement

(a) 11101010
 Sol:- 1's Complement = convert 1's as 0's. and
 0's as 1's.

$$11101010 \Rightarrow 00010101$$

1's Complement = 00010101.

\Rightarrow 2's Complement = Add 1 to 1's Complement.

$$\begin{array}{r} 00010101 \\ + 1 \\ \hline 00010110 \end{array}$$

$$(b) 0150 - 2100$$

$$\text{Sol:- } N = 2100; \gamma = 10; n = 4$$

$$= 10^4 - 2100$$

$$= 10,000 - 2100$$

\Rightarrow 10's Complement

$$\text{Step-2:- } M + \gamma(N) = \text{sum}$$

$$M = 0150$$

$$\begin{aligned} \text{10's Complement } N &= 7900 \\ &= 8050 \end{aligned}$$

$$\text{Step-3:- } \gamma\text{'s of sum}$$

$$\gamma\text{'s} = \gamma^n - N$$

$$= 10^4 - 8050$$

$$= 10,000 - 8050$$

$$= 1,950$$

$$\boxed{M > N}$$

(6) Perform subtraction on the Unsigned no's Using
2's Complement.

$$(a) 11011 - 11001$$

$$\begin{array}{r} x \\ \times \\ 11011 \\ - 11001 \\ \hline \end{array}$$

1's Complement

$$\begin{array}{r} 11001 - 00110 \\ + 1 \\ \hline 00111 \rightarrow 2\text{'s Complement} \end{array}$$

$$\begin{array}{r} 00000 \\ y 00111 \\ x 11011 \\ \hline 1000000 \end{array}$$

$$1,00,010 - 00010$$

(b) $101010 - 101011$

solve

$$101011 = \begin{array}{r} 010100 \\ + 1 \\ \hline 010101 \end{array} \rightarrow \text{2's Complement}$$


$$y = 010101$$

$$x = \begin{array}{r} 101010 \\ \hline 111111 \end{array}$$

$$\text{sum} = 111111 \rightarrow \text{no end carry}$$

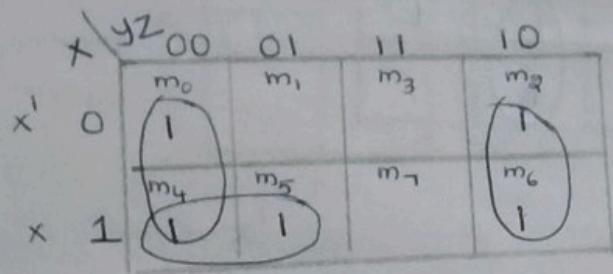(1)

$$(i) (x, y, z) = \Sigma(0, 2, 4, 5, 6)$$




$$A = z'$$

$$B = xy'$$

$$f(x, y, z) = xy' + z'$$

$$(ii) F = A'C + A'B + ABC' + BC \text{ express in sum of m}$$

terms.

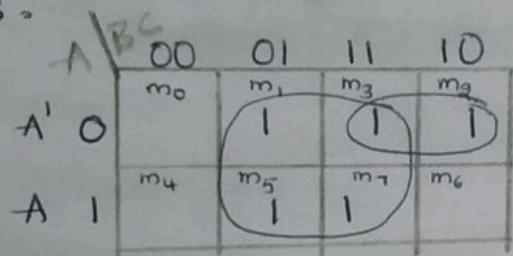

$$\neg A = C$$


$$B = A'B$$

$$F(A, B, C) = \Sigma(1, 2, 3, 5, 7)$$

$$= \neg A'B + C$$

(iii)

$$F(x, y, z) = \Sigma(0, 2, 6, 7)$$

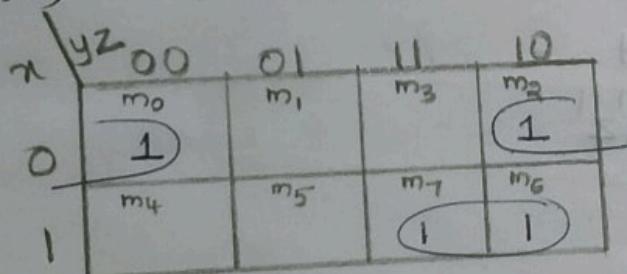

$$A = xz'$$

$$B = xy$$

$$F(x, y, z) = xy + xz'$$

$$(iv) F(a, b, c) = \sum (0, 1, 2, 3, 7)$$

a\bc	00	01	11	10
0	1	1	1	1
1			1	

$$A = a'$$

$$B = bc$$

$$F = a' + bc$$

$$(v) F(A, B, C) = \sum (0, 2, 3, 4, 6)$$

A\BC	00	01	11	10
0	1		1	1
1	1			1

$$A = C'$$

$$B = A'B$$

$$F = A'B + C$$

$$(vi) xy + x'y'z' + x'yz'$$

x\yz	00	01	11	10
0	1			1
1			1	1


$$A = x'z'$$

$$B = xy$$

$$F = xy + x'z'$$

(VII)

$$x'y' + yz + x'y'z'$$

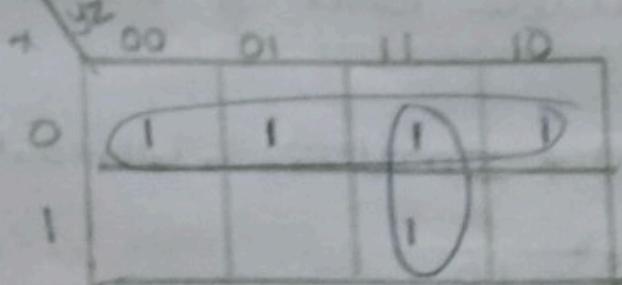


$$\neg A = x'$$

$$B = yz$$

$$F = x' + yz$$

(VIII)

$$A'B + BC' + B'C'$$

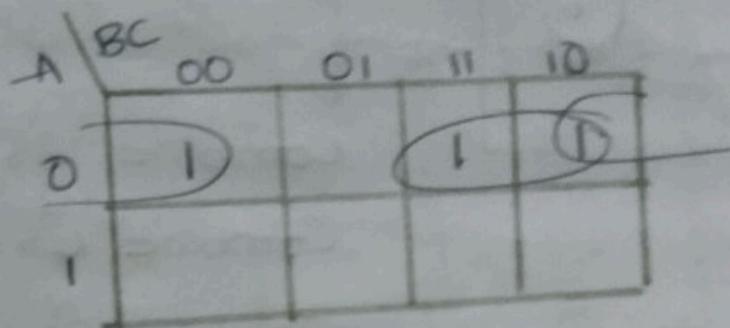

$$\neg A = A'C'$$


$$B = A'B$$

$$F = A'B + A'C'$$

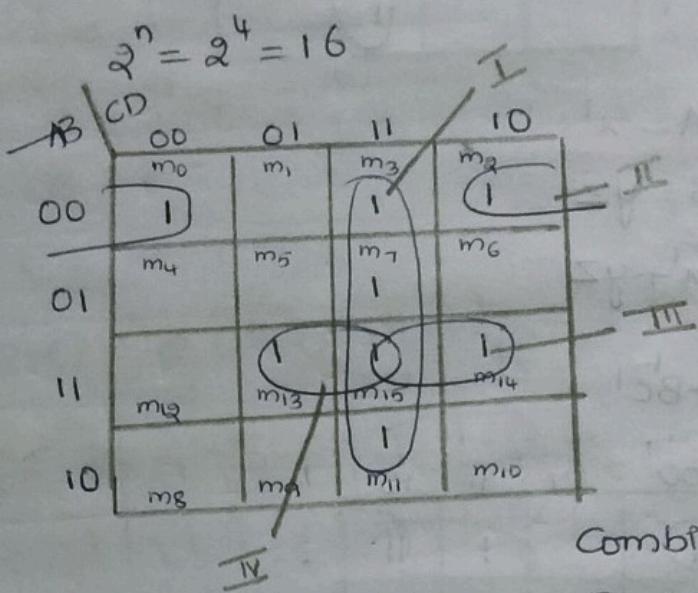(1)

Explain 4 variable and 3 variable K-map with explain.

$$\text{Ex :- } F(A, B, C, D) ; \Sigma m(0, 2, 3, 7, 11, 13, 14, 15)$$



Combine 2's \rightarrow Literal is 1

Combine 4's \rightarrow 2 literal

Combine 8's \rightarrow 3 literal


Combine 16's \rightarrow 4 literal

$$f = I + II + III + IV$$

$$= CD + A'BD' + ABC + ABD$$

3 variable :-

$$-A'B'C + A'BC + ABC' + ABC$$

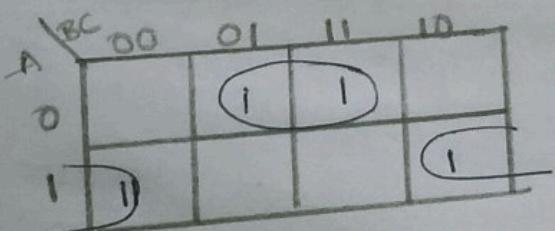

$$F = I + II$$

$$= AC + AC'$$

(2) Explain Don't care Condition with example-

Sol:- $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$

$d(wxyz) = \Sigma(0, 2, 5) = d$

d (or) \times symbol

→ sum of product $x = 1$

→ product of sum $x = 0$

→ Large group

→ Reduce taking don't care in a group

w\z	00	01	11	10
00	x	1	1	x
01	x	1	1	
11			1	
10			1	



$$y = yz + w'x' \rightarrow zx$$

$$y = yz + w'z$$

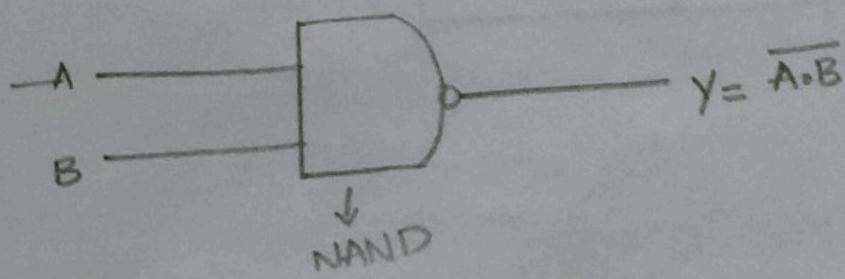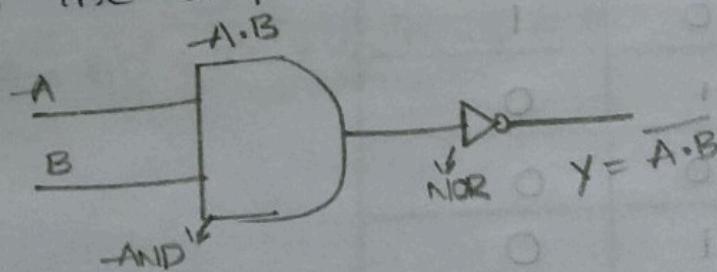(3) Explain NAND and NOR circuits.

Sol:- NAND gate :- NAND gate it is a combination of AND & NOT gates. It has two or more inputs & only one output.



→ When all the input are 'HIGH' the output is 'LOW' if any one or both input are 'LOW' then the output is 'HIGH'.



Truth table :-

Input		Output
A	B	$y = \overline{A+B}$
0	0	1
0	1	1
1	0	1
1	1	0

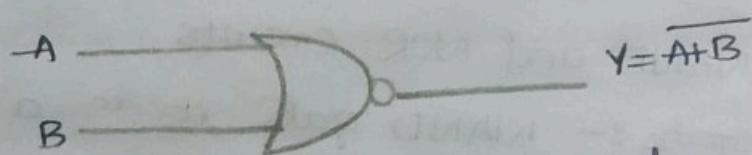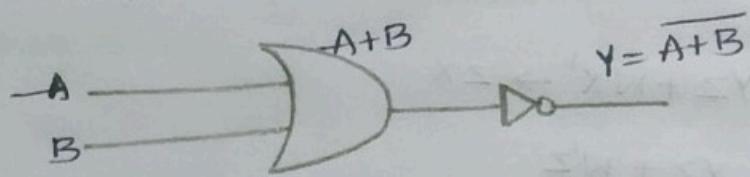NOR Gate - It is a combination of NOT and OR gate. It has two or more input only one output. The output is "HIGH" only when all the input are "LOW". If one or both input are "HIGH" then the output is "LOW".



NOR gate symbol

Truth table

Input		Output
A	B	$y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

(4) Simplify sum of products and products of sum problem.

sum of product (SOP) \rightarrow sum = +

product of sum (POS) \rightarrow product = x

3 Variable :- A, B, C

$$\rightarrow (AB) + (BC)$$

4 Variable :- A, B, C, D

$$Eg: -(ABC) + (BCD) + (CDA) \rightarrow \text{standard form}$$

$$(A'B'CD) + (AB'C'D) + (ABC'D') + (ABC'D) \rightarrow \text{Canonical}$$

\downarrow
Sum of product

All forms are involved.

Product of sum :- (POS)

Eg:- 3 variable (A, B, C)

$$(A+B) \cdot (B+C) \rightarrow \text{standard product of sum}$$

$$(A'+B+C)(A+B'+C)(A+B+C') = \text{Canonical product of sum.}$$

sum of product Examples-

$$F(A, B, C, D) = ? (0, 2, 5, 8, 9, 10).$$

		CD	00	01	11	10
AB	00	1	1			1
	01					
11	00					
	01	m ₁₂	m ₁₃	m ₁₅	m ₁₄	
10	00	1	1			1
	01	m ₅	m ₉	m ₁₁	m ₁₀	

$$F = B'D' + B'C' + A'C'D \rightarrow \text{SOP}$$

product of sum :-

AB\CD	00	01	11	10
00				
01	0			0
11	0	0	0	0
10				

$$R' = \neg AB + BD + CD$$

By using demorgan's law

$$(A+B)' = A'B$$

$$P' = (\neg AB + CD + BD)'$$

$$P = (\neg AB)' + (CD)' + (BD)'$$

$$= (A'+B') \cdot (C'+D') \cdot (B'+D')$$

↓ product of sum

(1) Explain (or) Define Combination Circuit.

Sol:- Combination Circuit

(1) Half adder

(2) Full adder

(3) Multiplexer

2:1

4:1

8:1

16:1

(4) Demultiplexer

1:2

1:4

1:8


1:16

(5) Encoders

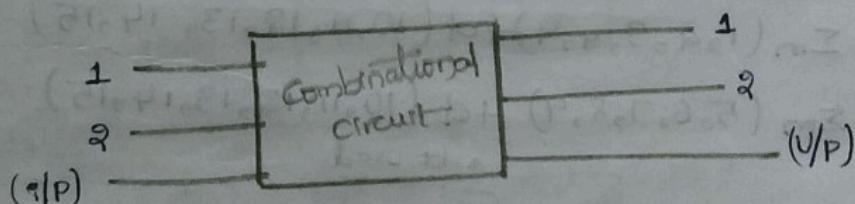(6) decoders

Combinational Circuit :-

- * The output of the circuit depends upon the combination of input variables.
- * It is a logic circuit having gates inbuilt (OR) integrated in it.
- * It doesn't use any memory.
- * 'n' number of inputs, 'm' no. of outputs.



It does not use any memory.

It depends on present input.

* It design with logic gates. It does not depend on previous inputs only depends on present inputs is called Combinational Circuit.

(2) Explain logic diagram for BCD-to excess-3 code converter.

Designing implementation

Decimal NO	BCD Code				Excess-3 code				
	B ₄	B ₃	B ₂	B ₁	X ₄	X ₃	X ₂	X ₁	
0	0	0	0	0	3	0	0	1	4
1	0	0	0	1	4	0	1	0	0
2	0	0	1	0	5	0	1	0	1
3	0	0	1	1	6	0	1	1	0
4	0	1	0	0	7	0	1	1	1
5	0	1	0	1	8	1	0	0	0
6	0	1	1	0	9	1	0	0	1
7	0	1	1	1	10	1	0	1	0
8	1	0	0	0	11	1	0	1	1
9	1	0	0	1	12	1	1	0	0


$$X_1 = \sum_m (0, 2, 4, 6, 8) + \text{don't care } (10, 11, 12, 13, 14, 15)$$

min term

$$X_2 = \sum_m (0, 3, 4, 7, 8) + \text{d } (10, 11, 12, 13, 14, 15)$$

$$X_3 = \sum_m (1, 2, 3, 4, 9) + \text{d } (10, 11, 12, 13, 14, 15)$$
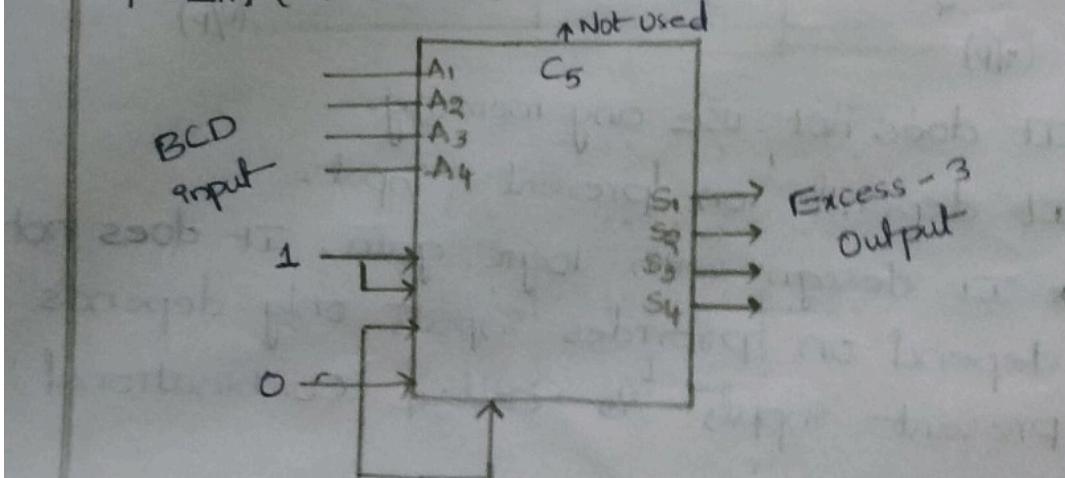
$$X_4 = \sum_m (5, 6, 7, 8, 9) + \text{d } (10, 11, 12, 13, 14, 15)$$



BCD-to excess-3 Code Converter

K-Map

$$X_1 = \sum_m(0, 2, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$$

$B_3 B_2$	$\bar{B}_3 B_2$	00	01	11	10
00	1	0	0	1	
01	1	0	0	1	
11	X	X	X	X	
10	1	0	X	X	

$X_1' = \bar{B}_3 B_2$

Σ_{map} for X_2

$$X_2 = \sum_m(0, 3, 4, 7, 8) + d(10, 11, 12, 13, 14, 15)$$

$B_3 B_2$	$\bar{B}_3 B_2$	00	01	11	10
00	1	1	X	1	
01	0	0	X	0	
11	1	1	X	X	
10	0	0	X	X	

$$\bar{B}_3 \bar{B}_2 + B_3 B_2$$

$$X_3 = \sum_m(1, 2, 3, 4, 9) + d(10, 11, 12, 13, 14, 15)$$

$B_3 B_2$	$\bar{B}_3 B_2$	00	01	11	10
00	0	1	X	0	
01	1	0	X	1	
11	1	0	X	X	
10	1	0	X	X	

$$\bar{B}_3 \bar{B}_2 \bar{B}_1 + \bar{B}_3 B_2 B_1 + \bar{B}_3 B_2$$

$$X_4 = \sum_m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

$B_3 B_2$	$\bar{B}_3 B_2$	00	01	11	10
00	0	0	X	1	
01	0	1	X	1	
11	0	1	X	X	
10	0	1	X	X	


$$B_4 + B_3 B_2 + B_3 B_2$$

$$X_1 = \overline{B}_1$$

$$X_2 = \overline{B}_2 \overline{B}_1 + B_2 B_1$$

$$X_3 = \overline{B}_3 \overline{B}_2 \overline{B}_1 + \overline{B}_3 B_2 B_1 + \overline{B}_3 B_2$$

$$X_4 = B_4 + B_3 B_1 + B_3 B_2$$

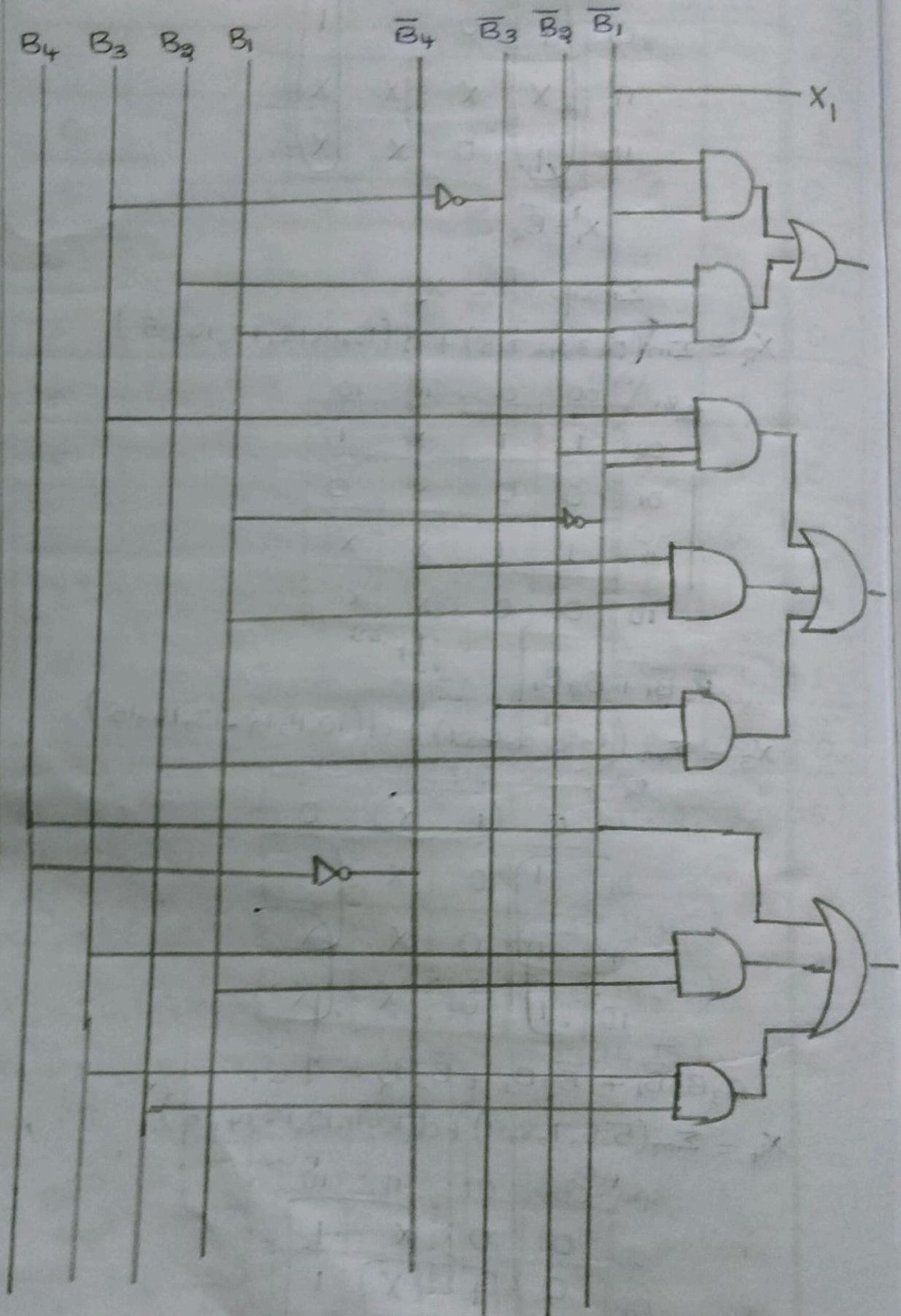


(3) Explain half-adder and full-adder with an example.

Half-adder

Designed to add single bit number


It has two inputs and two outputs

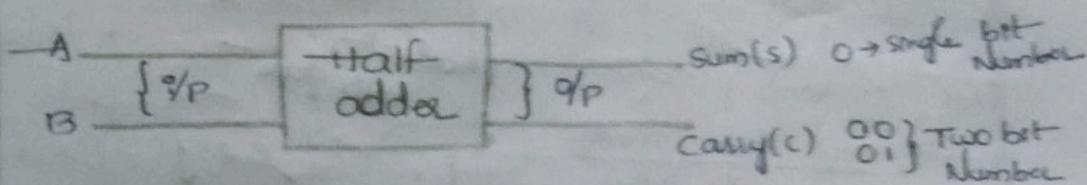

D+O(OR) GATE


Truth table

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

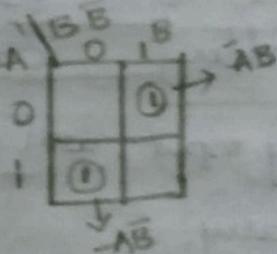

$$= \bar{A}\bar{B} + \bar{A}B$$


Sum:-

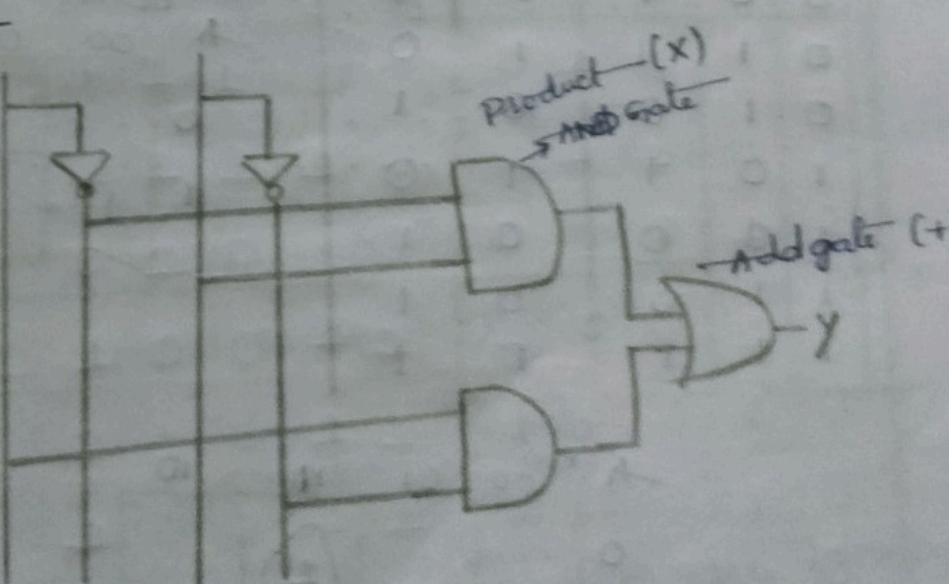

* Carry


	B	0	1
0	0	0	0
1	1	1	1

① AB

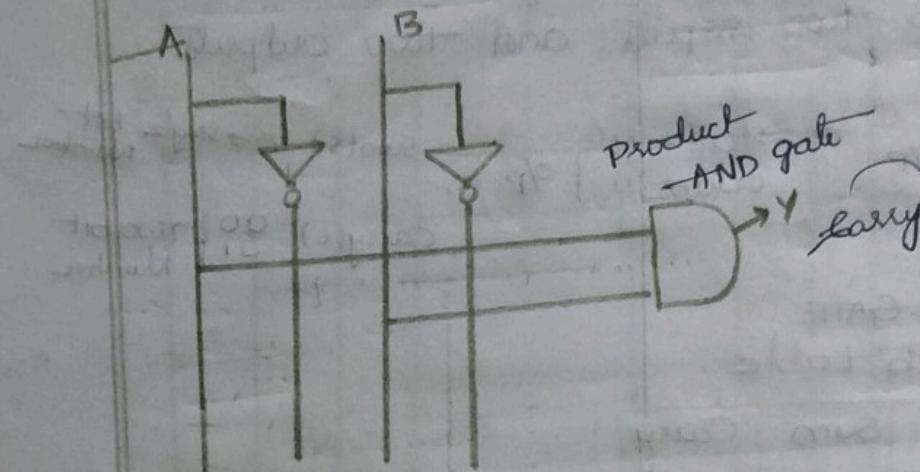

* Full adder :-

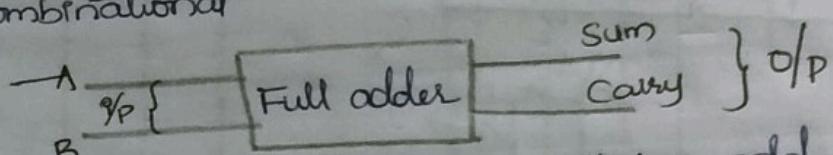→ It is designed to add two single bit numbers with a Carry (or) Arithmetic logical Combinational



Cin → Carry input will be odd.

A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	1	1	0
0	1	0	0	1
1	0	1	1	0
1	0	0	0	1
1	1	0	0	1
1	1	1	1	1

A		B Cin		
00	01	11	10	
0	1	1	1	
1	1	1	1	


A		B Cin		
00	01	10	11	
0	1	1	1	
1	1	1	1	

Cin A

BA

$$B_{\text{Cin}} + BA + \text{Cin}A$$

* Logic diagram:-

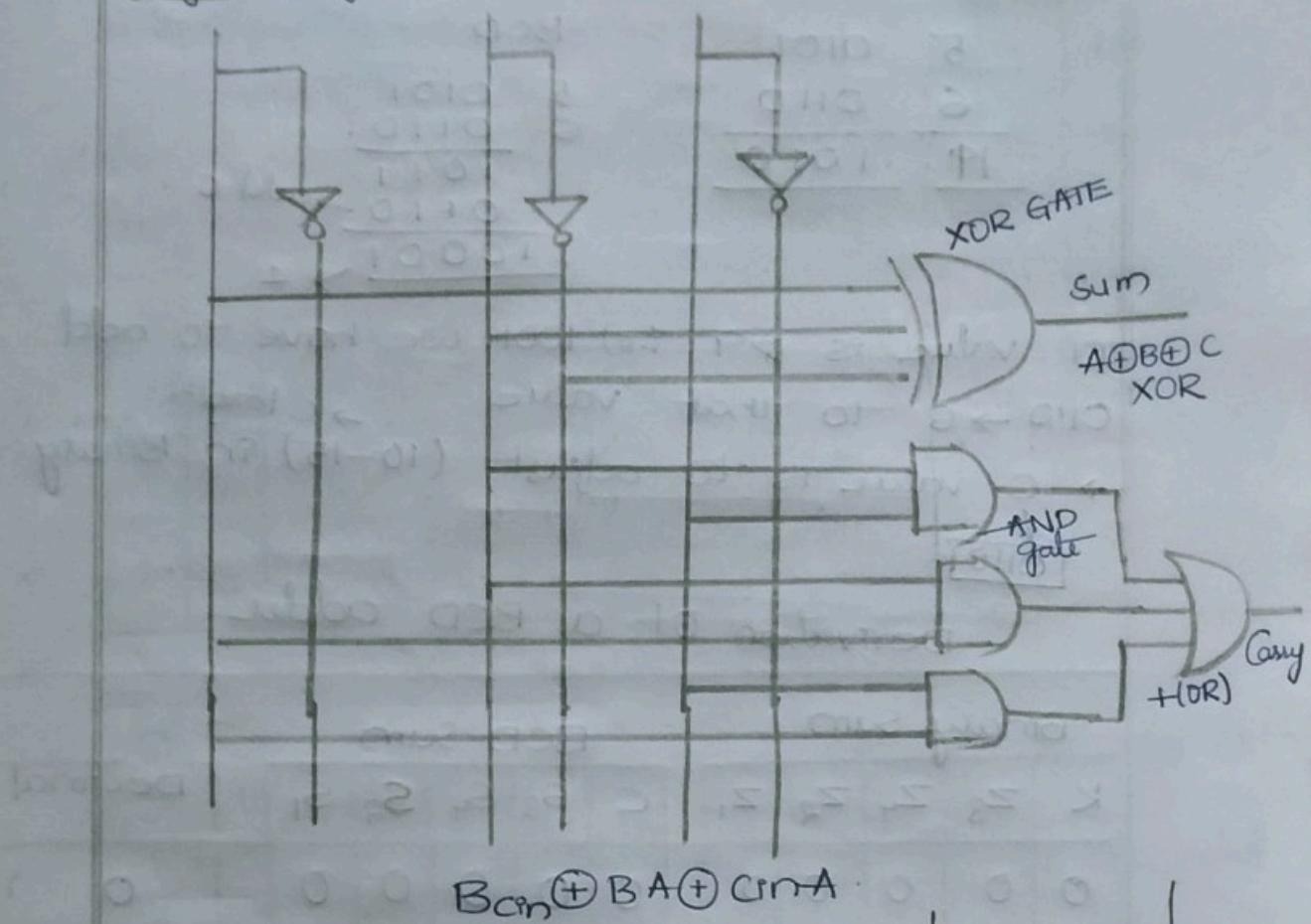

$$B_{\text{cin}} \oplus B_A \oplus C_{\text{in}} - A$$

(4) Explain BCD adder with an explain example diagram.

Sols:- Adding 4 bit BCD code

- * In 4 bit we have max. value upto $9^{\rightarrow 1001}$
- * so, we can add max value up to $9+9+1$.
- 1 is the Input Carry.

$$\begin{array}{r} \cancel{9} + \cancel{9} + 1 = 19 \\ \text{Addend} \quad \text{Augend} \end{array}$$

- * BCD Addition and binary addition are same up to 9 \rightarrow from 0 to 1 being

Case-1 :- Total is less than or equal to 9.

$$\begin{array}{r} 1 \rightarrow 0001 \\ 5 \rightarrow 0101 \\ \hline 6 \rightarrow 0110 \end{array}$$

Up to 9 $\rightarrow 1001$ both BCD are binary are going to be same.

Case-2: total is >9

$$\begin{array}{r} 5 \\ 6 \\ \hline 11 \end{array} \quad \begin{array}{r} 0101 \\ 0110 \\ \hline 1010 \end{array}$$

BCD

$$\begin{array}{r} 5 \\ 6 \\ \hline 1011 \\ 0110 \\ \hline 10001 \end{array} \rightarrow 1$$

add 6

If value is >9 i.e) 1001 we have to add
 $0110 \rightarrow 6$ to that value $\xrightarrow{\text{length}} 6$
 \rightarrow 6 value is to adjust $(10-15)$ in Binary
 \downarrow
 $\boxed{0110}$

Derivation of a BCD adder

Binary sum					BCD sum					Decimal
K	z_8	z_4	z_2	z_1	C	s_8	s_4	s_2	s_1	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	1	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12

K	Z_8	Z_4	Z_2	Z_1
0	1	1	0	1
0	1	1	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1

C	S_8	S_4	S_2	S_1	
1	0	0	1	1	13
1	0	1	0	0	14
1	0	1	0	1	15
1	0	1	1	0	16
1	0	1	1	1	17
1	1	0	0	0	18
1	1	0	0	1	19

→ From truth-table

If $C=0$ Comes Under Case 1 so no change is required.

If $C=1$ Comes Under case 2 we have to add 0110 to the output.

To find the relation we have to find Boolean function.


Z_8	Z_4	Z_2	Z_1	
00	01	11	10	
00				
1	1			
1	1	1	1	

$K=0$

Z_8	Z_4	Z_2	Z_1	
00	01	11	10	
00				
d	d	d	d	
d	d	d	d	
d	d	d	d	


$K=1$

$$C = K + Z_8 Z_4 + Z_8 Z_2$$

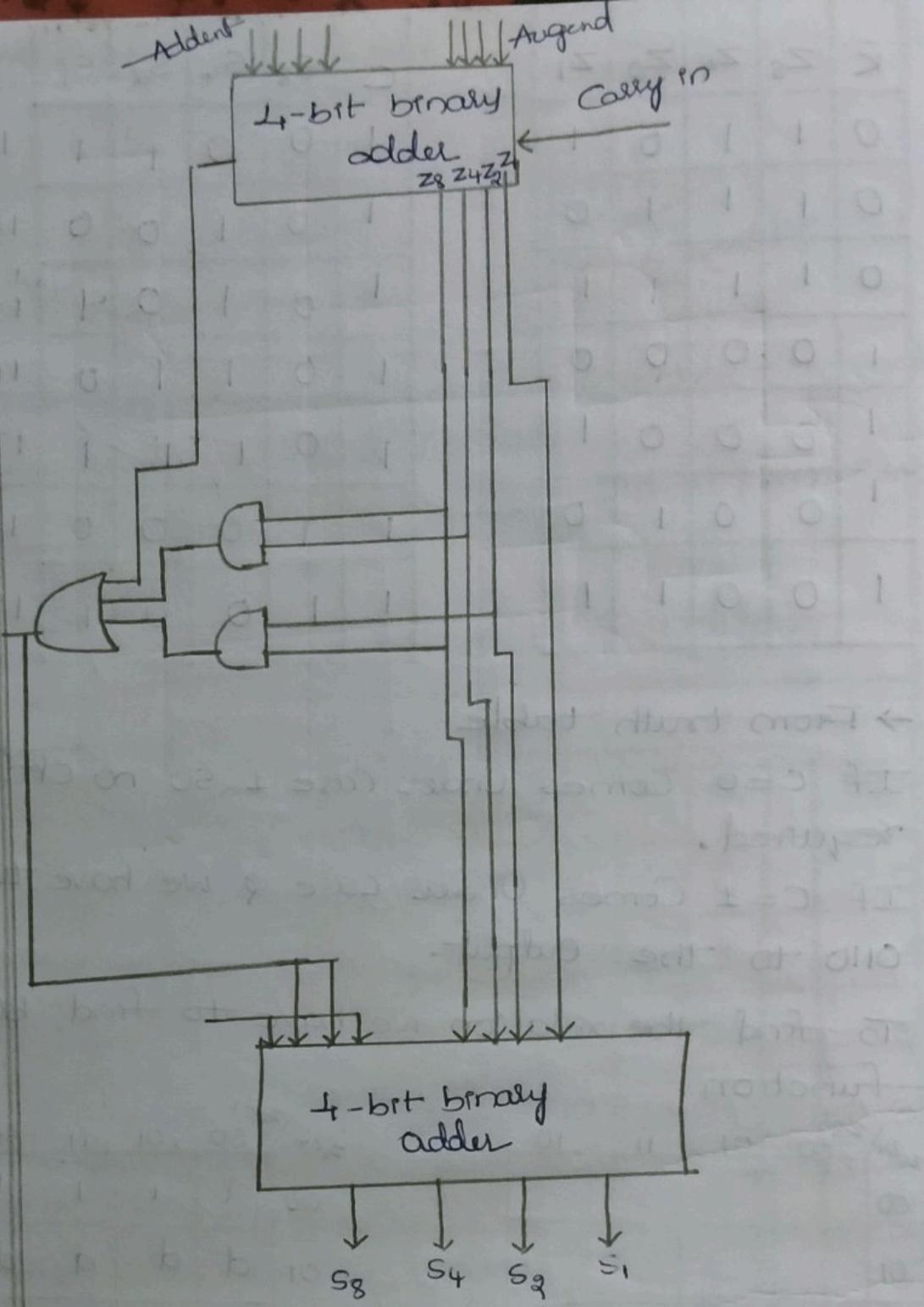

→ BLOCK DIAGRAM OF A BCD-ADDER

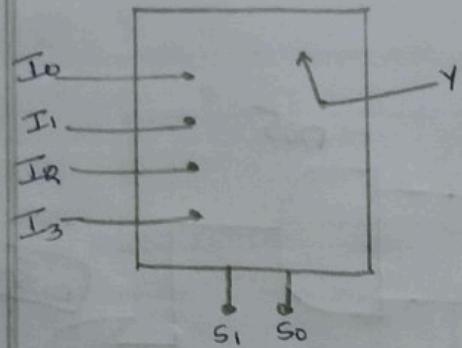(5) Explain binary multiplexer with example.



$m = 2 \rightarrow$ select
 $\therefore P. m = 2^2 = 4$ 2 line select
 $m = 4 \rightarrow$ inputs
 $m = 2^3 \rightarrow$ select line
 $= 8$ inputs
 $m = 2^4 \rightarrow$ select line
 $= 16$ inputs

Advantages:- Any input but 1 is output of depends upon selection lines (S)

- * Reduces no. of wires.
- * Reduces Complexity Cost.
- * MUX design implement various design.
- * Simplify the circuit it is not Complex.

Types of MUX :-

2:1 MUX


4:1 MUX

8:1 MUX

16:1 MUX


32:1 MUX

2:1 MUX

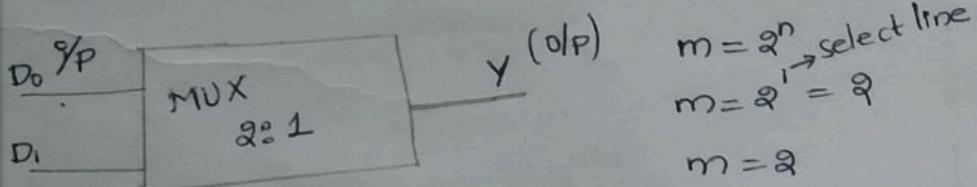


$m = 2^n \rightarrow$ select line
 $m = 2^1 = 2$
 $m = 2$

S	Y
0	D0
1	D1

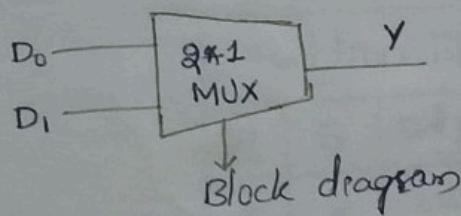


$$Y = D_0 \bar{S} + D_1 S$$

→ logic diagram

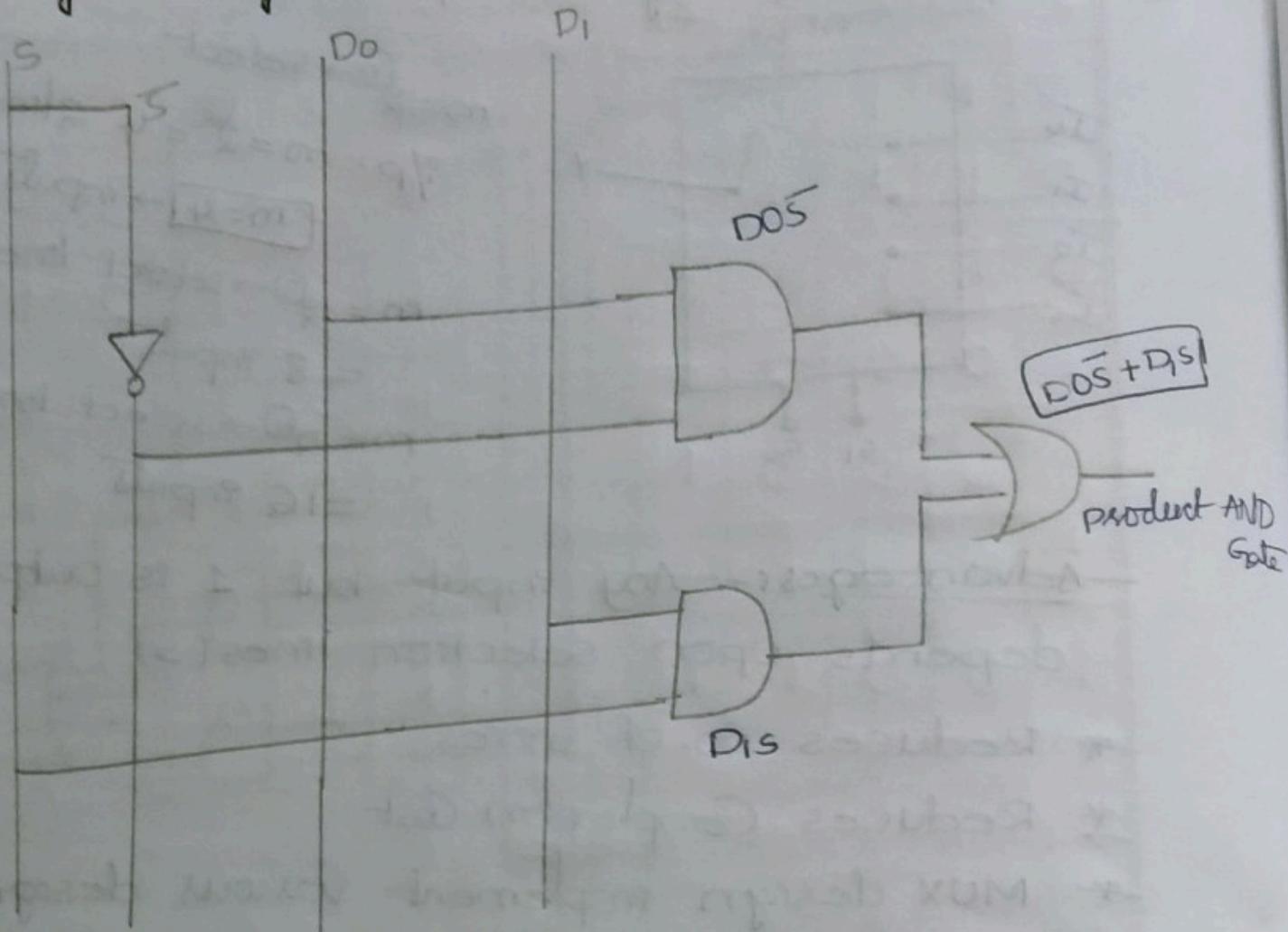

→ $2^* 1$ MUX diagram

(6) Explain 2-to-1 line multiplexers?

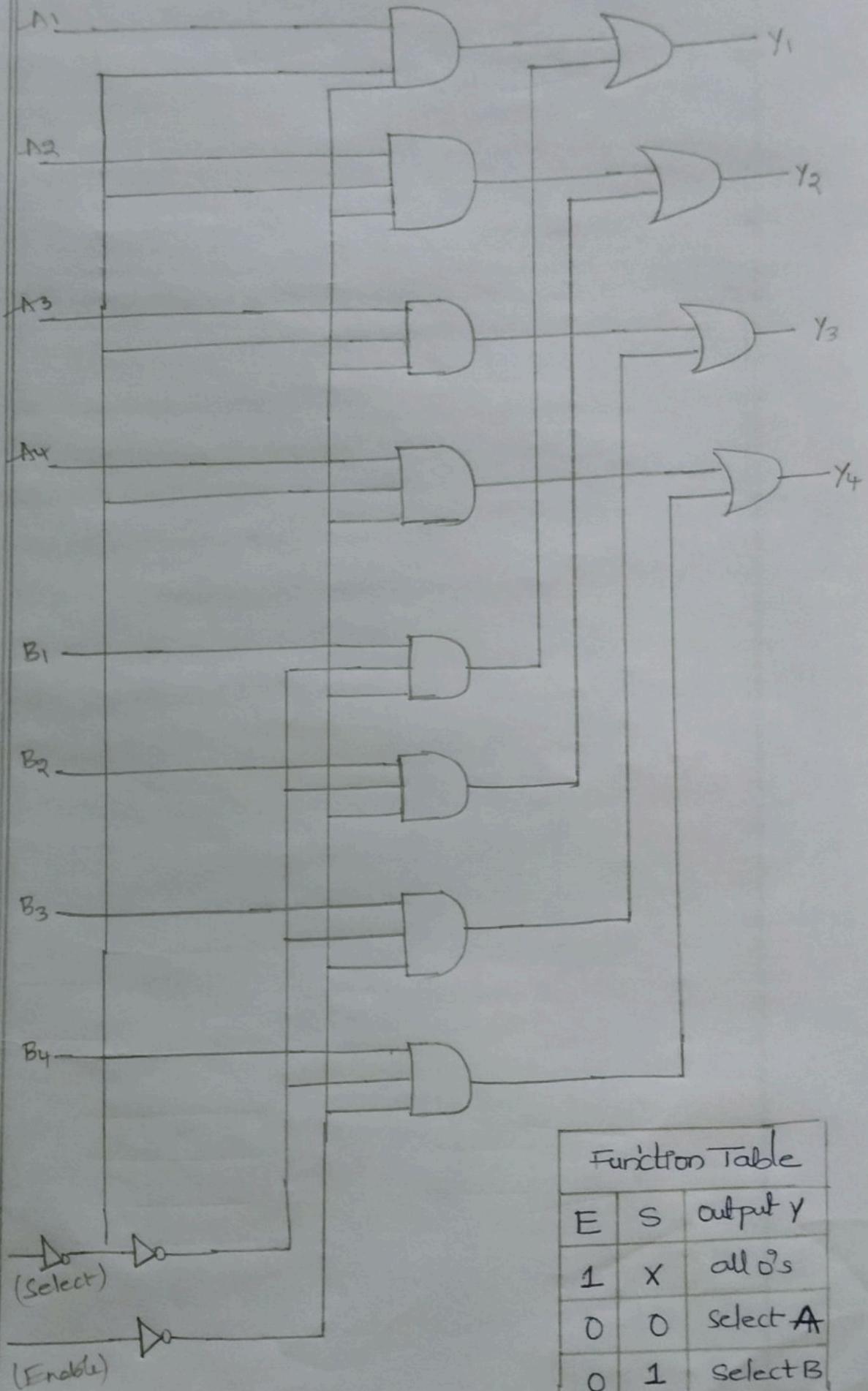

Function Table		
E	S	Output Y
1	X	all 0's
0	0	Select A
0	1	Select B

→ Quadiple - 2 to -1 line multiplexer.